

HANOI UNIVERSITY OF SCIENCE AND TECHNOLOGY  
SCHOOL OF ELECTRICAL AND ELECTRONIC ENGINEERING



## DESIGN SPECIFICATION

*LAB3*

### 7-segment Century Digital Clock

**Student:** Nguyen Phuong Linh

Ha Noi, May 2023

# Contents

List of Figures	2
List of Tables	2
1 Top module	3
2 Port description	3
3 Functional Descriptions	4
4 Timing Diagram	5

## List of Figures

1	TOP module . . . . .	3
2	Timing Diagram of top module . . . . .	5
3	Timing Diagram of clk_1hz (generate 1hz clk from 50MHx clk) module . . . . .	5
4	Timing Diagram of counter module . . . . .	5
5	Timing Diagram of count and display seconds/minutes module . . . . .	6
6	Timing Diagram of count and display hours module . . . . .	6
7	Timing Diagram of count and display months module . . . . .	6
8	Timing Diagram of count and display years module . . . . .	6

## List of Tables

1	Port description of top module . . . . .	4
---	--	---

## 1 Top module

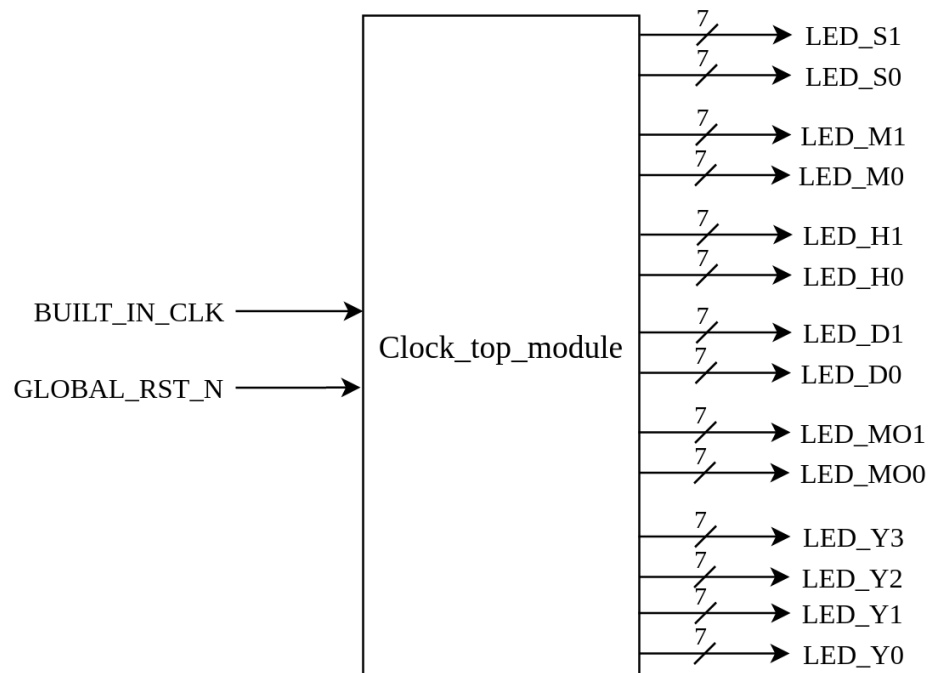


Figure 1: TOP module

I modularized the top module into smaller modules to count and display seconds, minutes, hours, days, months and years separately. The waveform for those module will be provide in **appendix A**.

## 2 Port description

Signal name	Width	I/O	Description
BUILT_IN_CLK	1	Input	Built-in clock (50MHz) of DE2-115 FPGA Board
GLOBAL_RST_N	1	Input	Global reset active low (hard reset)
LED_S1	7	Output	Decode tens of seconds
LED_S0	7	Output	Decode units of seconds
LED_M1	7	Output	Decode tens of minutes
LED_M0	7	Output	Decode units of minutes
LED_H1	7	Output	Decode tens of hours
LED_H0	7	Output	Decode units of hours
LED_D1	7	Output	Decode tens of days
LED_D0	7	Output	Decode units of days
LED_MO1	7	Output	Decode tens of months
LED_MO0	7	Output	Decode units of months
LED_Y3	7	Output	Decode thousands of years
LED_Y2	7	Output	Decode hundreds of years
LED_Y1	7	Output	Decode tens of years
LED_Y0	7	Output	Decode units of years

Table 1: Port description of top module

### 3 Functional Descriptions

- BUILT\_IN\_CLK is provided to the module, then is divided to 1Hz clock for all module
- When clock starts counting: 2 LED LED\_S1 and LED\_S0 which display seconds increasing over real-time. When it reaches 10, LED\_S0 (represents units of seconds) returns to 0, and LED\_S1 light for the tens of seconds increases by 1 unit. When it reaches 6, LED\_S1 which represents tens of seconds returns to 0, and the LED\_M0 (the units of minutes) increases by 1 unit.
- 2 LED LED\_M1 and LED\_M0 behave similar with LED\_S1 and LED\_S0.

- When 2 LED represent hours display 24, they both return to 0, and LED\_D0 will increase by 1 unit. When it reaches 10, it returns to 0, and LED\_D1 increases by 1 unit. Similarly with 2 LEDs represent months and 4 LEDs represent years

## 4 Timing Diagram

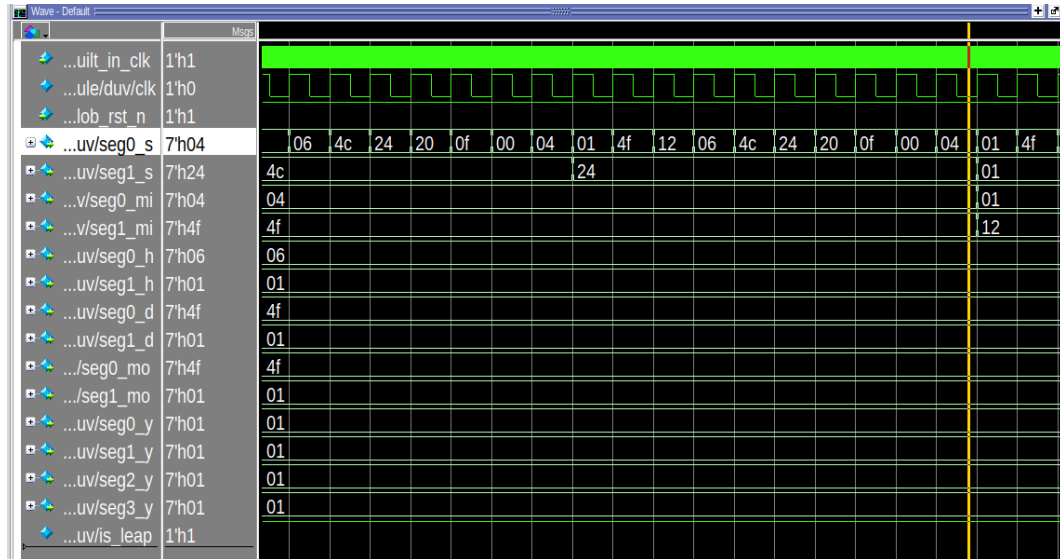


Figure 2: Timing Diagram of top module

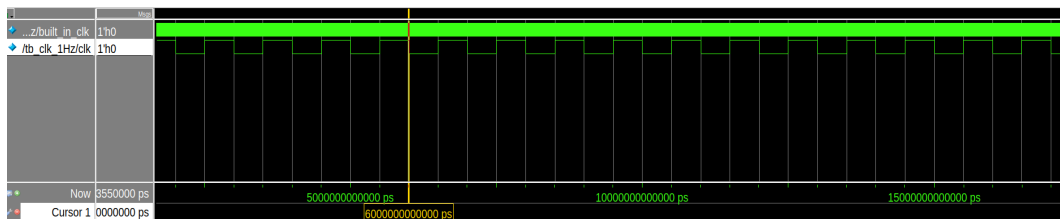


Figure 3: Timing Diagram of clk\_1hz (generate 1hz clk from 50MHx clk) module

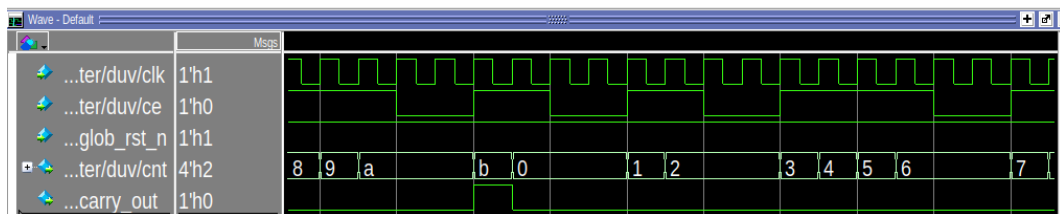


Figure 4: Timing Diagram of counter module

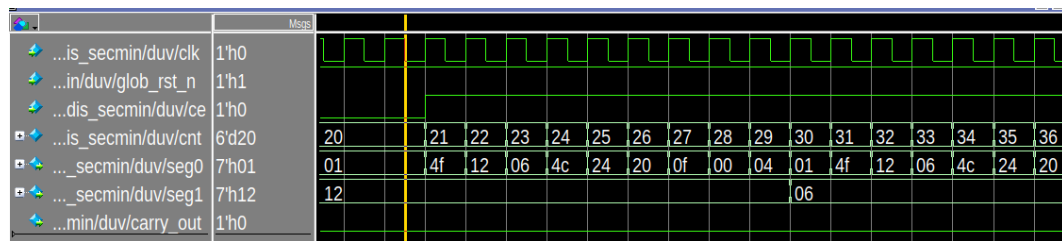


Figure 5: Timing Diagram of count and display seconds/minutes module

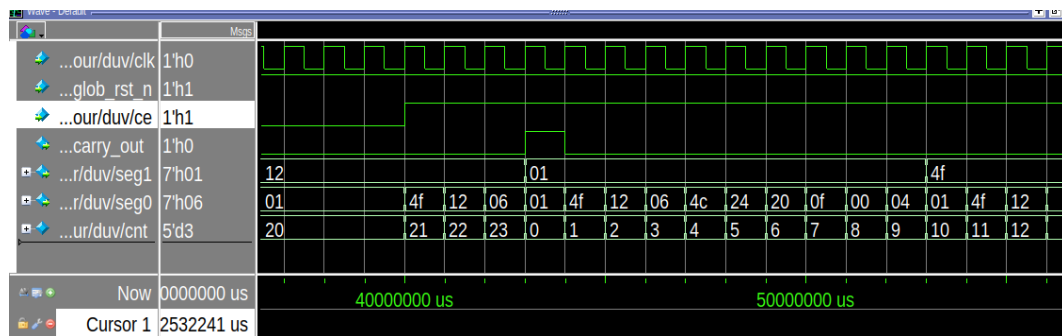


Figure 6: Timing Diagram of count and display hours module

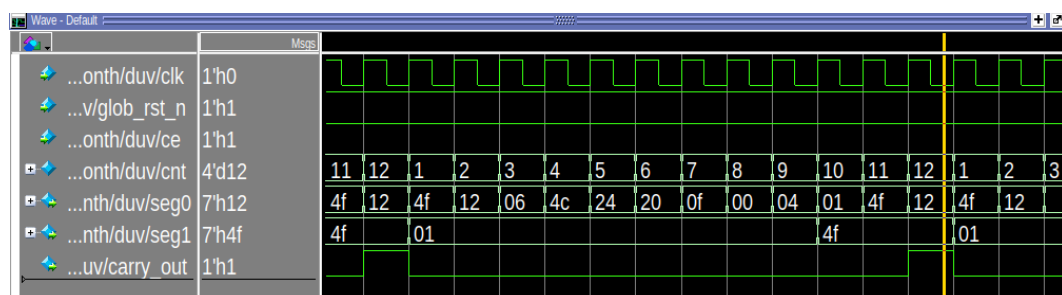


Figure 7: Timing Diagram of count and display months module

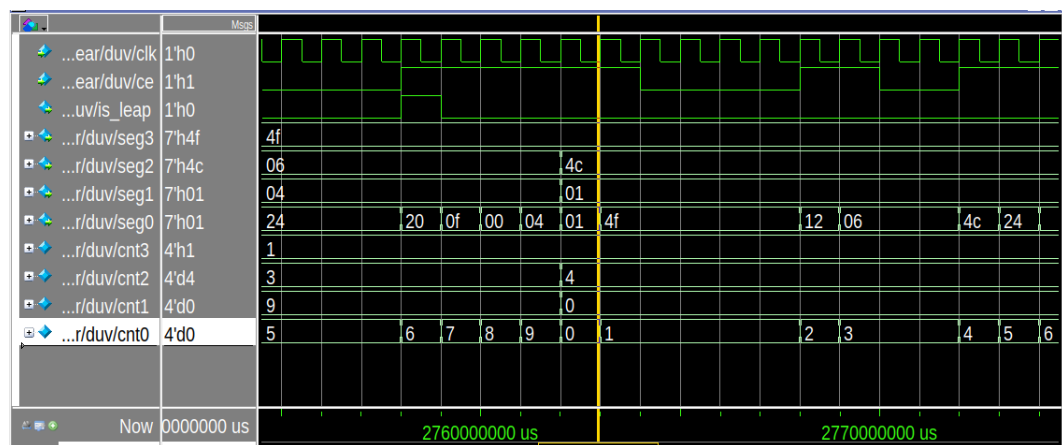


Figure 8: Timing Diagram of count and display years module