

HANOI UNIVERSITY OF SCIENCE AND TECHNOLOGY  
SCHOOL OF ELECTRICAL AND ELECTRONIC ENGINEERING



## DESIGN SPECIFICATION

*LAB4*

### Traffic Light Highway - Country Control System

**Student:** Nguyen Phuong Linh

Ha Noi, May 2023

# Contents

List of Figures	2
List of Tables	2
1 Top module	3
2 Port description	3
3 Functional Descriptions	3
4 Timing Diagram	4
A Block Diagram	4
B FSM Diagram	5

## List of Figures

1	TOP module . . . . .	3
2	Timing Diagram of top module . . . . .	4
3	Block Diagram of the system . . . . .	4
4	FSM Diagram for submodule control highway's traffic light . . . . .	5
5	FSM Diagram for submodule control country's traffic light . . . . .	5

## List of Tables

1	Port description of top module . . . . .	3
---	--	---

## 1 Top module

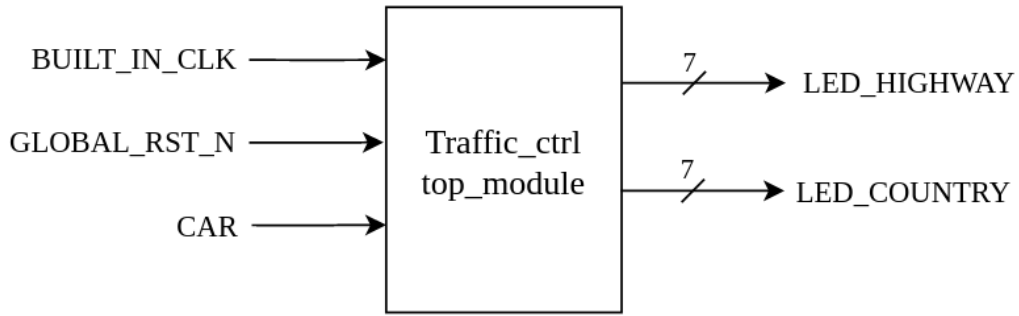


Figure 1: TOP module

I modularized the top module into smaller modules: timer (to count from 0 to t second when receive start signal), highway (module to control led in highway), country (module to control led in country). The block diagram is mentioned in **appendix A**.

## 2 Port description

Signal name	Width	I/O	Description
BUILT_IN_CLK	1	Input	Built-in clock (50MHz) of DE2-115 FPGA Board
GLOBAL_RST_N	1	Input	Global reset active low (hard reset)
CAR	1	Input	Signal from sensor (HIGH if there are cars in country road)
LED_HIGHWAY	7	Output	7-segment LED represents highway's traffic light: 0 = Green, 1 = Yellow, 2 = Red
LED_COUNTRY	7	Output	7-segment LED represents country's traffic light: 0 = Green, 1 = Yellow, 2 = Red

Table 1: Port description of top module

## 3 Functional Descriptions

- The highway is prioritized: always keeps Green when there is no car in country road. Country road's light always keeps Red
- If there are cars in country road:
  - **CAR** will be set HIGH, then traffic light in highway will be Green in T (seconds) then turns into Yellow in t (seconds) and finally turns into Red.

- When traffic light in highway turns into Red, the light in country road turns Green at the same time and stays Green for  $T$  (seconds).
- After that, country road's traffic light turns into Yellow in  $t$  (seconds) and finally turns back to Red.
- When traffic light in country turns into Red, the light in country road turns Green at the same time and repeats the process.
- For testing in FPGA, we decode states of traffic lights, are displayed by 7 segment LEDs **LED\_HIGHWAY** and **LED\_COUNTRY**:
  - 0 = Green
  - 1 = Yellow
  - 2 = Red

## 4 Timing Diagram

To verification the system , I use random input method. Figure 2 is simulated wave form at some specific time.

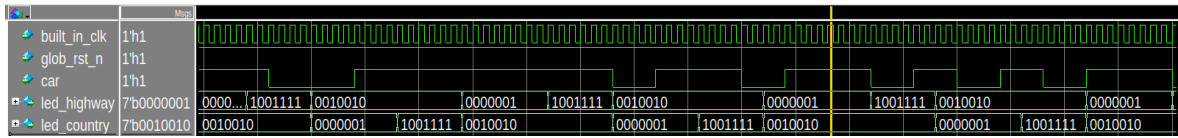


Figure 2: Timing Diagram of top module

## A Block Diagram

Figure 3 depicts how submodules interactive with each others in the system.

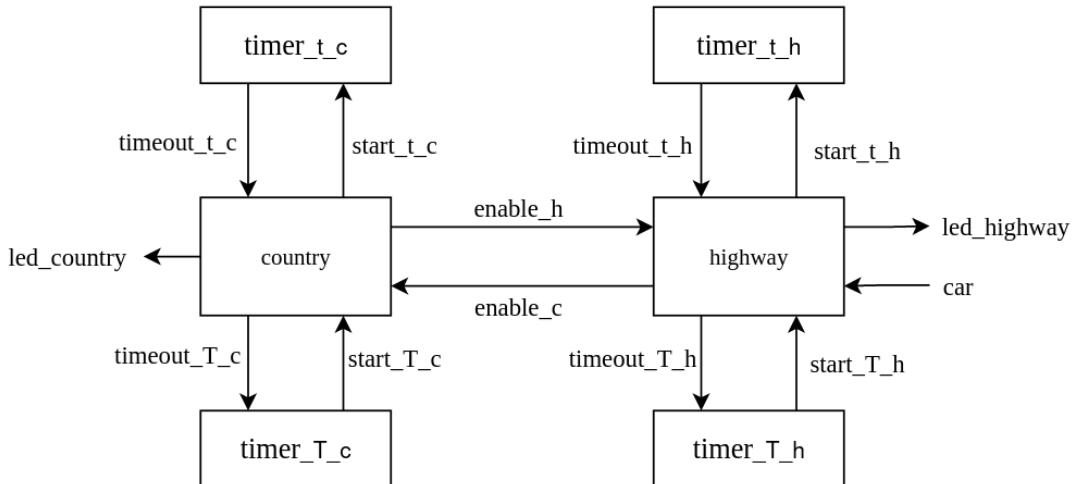


Figure 3: Block Diagram of the system

## B FSM Diagram

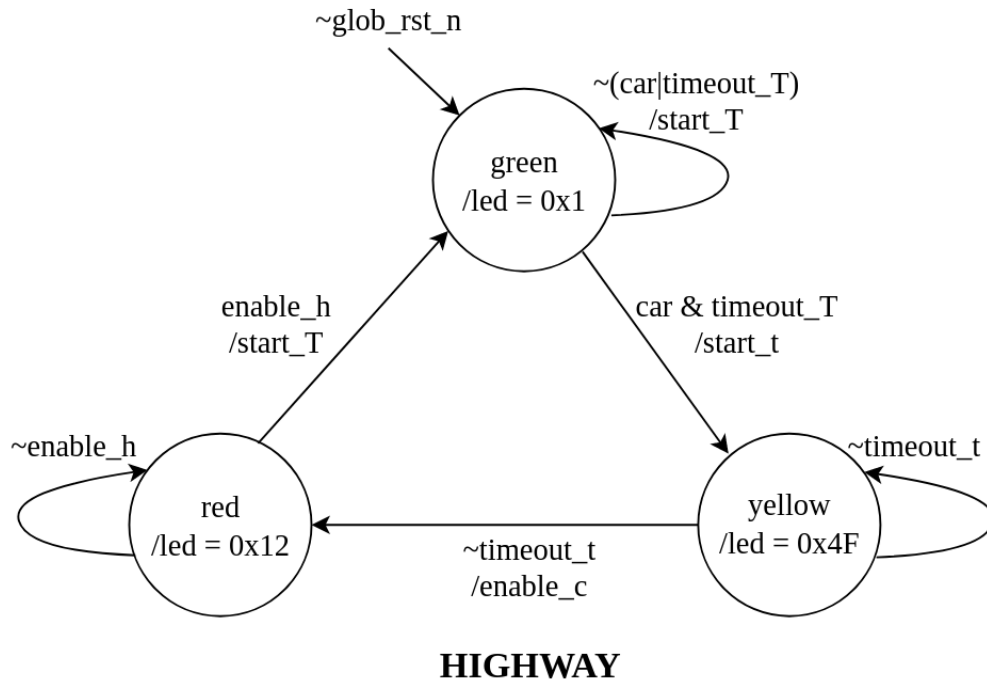


Figure 4: FSM Diagram for submodule control highway's traffic light

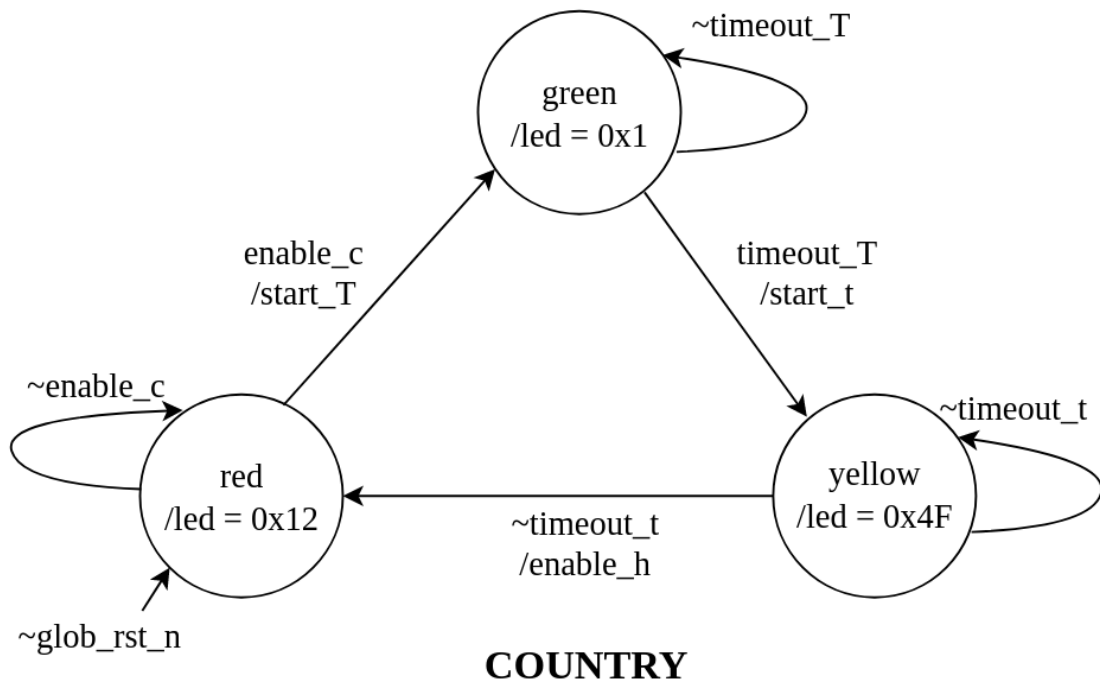


Figure 5: FSM Diagram for submodule control country's traffic light